


Visvesvaraya Technological University, Belagavi
MODEL QUESTION PAPER
3rd Semester, B.E (CBCS 2017-18 Scheme) EC/TC
Course: 17EC33- Analog Electronics, *Set no. 2*


Time: 3 Hours

Max. Marks: 100


Note: (i) Answer Five full questions selecting any one full question from each Module.

(ii) Question on a topic of a Module may appear in either its 1st or/and 2nd question.

 		Module-1	Marks
1	a)	Define h parameters and hence derive h parameters model of a CE BJT	5
	b)	Derive the expressions for A_I , A_V , Z_i and Z_o for a voltage divider bias circuit of BJT, Using re equivalent model of BJT. Show the phase relationship between input and output wave form.	10
	c)	What is Darlington Connection? Calculate the DC bias voltage and currents in the Darlington emitter follower circuit having $V_{CC}=18V$, $R_E=390\Omega$, $R_B=3.3M\Omega$, $V_{BE}=1.6V$ $\beta_D=8000$	5
			
		OR	
2	a)	Give the relation between re parameters and h parameters. What are the advantages of h parameters.	5
	b)	Derive the Expressions for current gain, voltage gain, input impedance and output impedance for an emitter follower circuit.	10


 
c)	<p>For the fixed bias network with $V_{CC}=15V$, $R_B=470K\Omega$, $R_C=4.7K\Omega$, $C_{C1}=C_{C2}=10\mu F$, $\beta=100$, $r_0=50K\Omega$</p> <p>a) Determine r_e, Z_i, Z_o, A_v (with $r_o=\infty\Omega$), A_v with $r_o=50K\Omega$</p> 	5
----	--	---

Module-2

 3	<p>a) Explain the construction of N channel JFET. Also explain the drain and transfer characteristics of the JFET.</p> <p>b) With Equivalent circuit obtain the expression for Z_o and A_v for JFET Self bias with unbypassed R_S.</p> <p>c) The fixed bias configuration shown in has $V_{GSQ}=-2V$, $I_{DQ}=5.625mA$ with $I_{DSS}=10mA$, $V_p=-8V$ and $Y_{OS}=40\mu S$, $V_{GG} = -2V$, $V_{DD}=20V$, $R_D=2K\Omega$, $R_G=2M\Omega$. Determine g_m, r_d, Z_o and A_v</p> 	6 8 6
---	--	-------------

OR

4	<p>a) Differentiate between Enhancement and Depletion MOSFET.</p> <p>b) With necessary equivalent circuit obtain the expression for Z_i and A_v for a JFET Common Gate configuration.</p>	6 8
---	---	--------

  	c)	<p>Calculate the DC bias, overall voltage gain. For the cascaded identical common source amplifier with $I_{DSS}=10\text{mA}$, $V_P=-4\text{V}$, $V_{DD}=20\text{V}$, $R_{D1}=R_{D2}=2.4\text{K}\Omega$, $R_{G1}=R_{G2}=3.3\text{M}\Omega$, $R_{S1}=R_{S2}=680\Omega$, $C_{S1}=C_{S2}=100\mu\text{F}$, $C_{C1}=C_{C2}=C_{C3}=0.05\mu\text{F}$.</p> 	6
Module-3			
5	a)	<p>The input power to a device is 10000W at a voltage of 1000V. The output power is 500W and the output impedance is 20Ω.</p> <p>i) Find the power gain in decibels. ii) Find voltage gain in decibels.</p>	5
	b)	<p>Discuss the low frequency response of BJT amplifier and give expression for lower cutoff frequency due to C_C, C_E and C_S.</p>	10
	c)	<p>Calculate the overall lower 3db and upper 3db frequencies for a 3 stage amplifier having an individual $f_1=40\text{Hz}$ and $f_2=2\text{MHz}$</p>	5
OR			
6	a)	<p>Discuss the effect of various capacitors in frequency response of an amplifier.</p>	5
	b)	<p>Determine the high cutoff frequencies for the common source amplifier, $C_G=0.01\mu\text{F}$, $C_C=0.5\mu\text{F}$, $C_S=2\mu\text{F}$, $R_{sig}=10\text{K}\Omega$, $R_G=1\text{M}\Omega$, $R_D=4.7\text{K}\Omega$, $R_S=1\text{K}\Omega$, $R_L=2.2\text{K}\Omega$, $I_{DSS}=8\text{mA}$, $V_P=-4\text{V}$, $r_d=\infty\Omega$, $V_{DD}=20\text{V}$</p> 	10
	c)	<p>Describe miller effect and derive an equation for miller input capacitance.</p>	5

Module-4			
7	a)	With block diagram explain the concept of feedback amplifier.	5
	b)	Derive the expression for Z_{if} and Z_{of} voltage series feedback amplifier.	5
	c)	For a practical current series feedback circuit derive expression for A_F and Z_{if} .	10
OR			
8	a)	What is an Oscillator? Discuss the concept of generating oscillations with the help of Barkhausen criteria.	5
	b)	Explain the operation of UJT Relaxation oscillator.	5
	c)	With a neat diagram and necessary expressions explain Hartley oscillator.	10
Module-5			
9	a)	Give the definition of power amplifier and list the types of power amplifier based on the location of Q point.	5
	b)	Explain the working of class B. Push pull amplifier. Obtain an expression for maximum conversion efficiency of this amplifier.	10
	c)	Calculate the harmonic distortion components for an output signal having fundamental amplitude of 2.5V, Second harmonic amplitude of 0.25V, third harmonic amplitude of 0.1 V and fourth harmonic amplitude of 0.05 V and also calculate the total harmonic distortion for the amplitude components given above.	5
OR			
10	a)	With necessary circuit diagram and characteristics curve, show that the maximum efficiency of a series fed class A amplifier is 25%.	10
	b)	Describe with block diagram the series and shunt type of voltage regulators.	5
	c)	Derive the voltage stability factor and output resistance for emitter follower series regulator.	5
