


Visvesvaraya Technological University, Belagavi
MODEL QUESTION PAPER – Set II
6th Semester, B.E (CBCS) EC
Course: 15EC655 - Microelectronics


Time: 3 Hours

Max. Marks: 80


Note: (i) Answer Five full questions selecting any one full question from each Module.
(ii) Question on a topic of a Module may appear in either its 1st or/and 2nd question.

MODULE 1

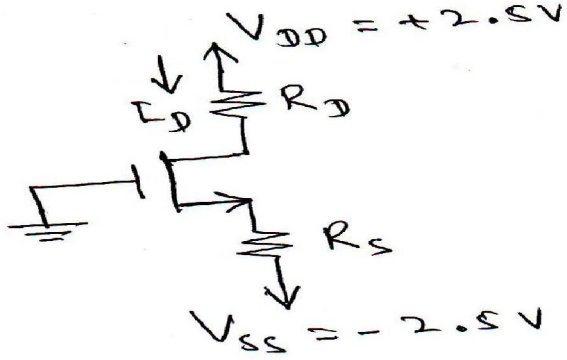1	a.	Derive the expression of drain current of a MOS device for triode and saturation region.	6 Marks
	b.	For the circuit shown in Fig. 1(b) has $I_D = 0.4\text{mA}$ and $V_D = 0.5\text{V}$. The NMOS transistor has $V_t = 0.7\text{V}$, $\mu_n C_{ox} = 100\mu\text{A/V}^2$, $L = 1\mu\text{m}$ and $W = 32\mu\text{m}$. Find the values of R_s and R_D . Assume $\theta = 0$.	6 Marks
	 <p style="text-align: center;">Fig. Q 1 (b).</p>		
c.	Mention the advantages of MOSFETs.	4 Marks	
OR			
2	a.	Explain the operation of enhancement type NMOS transistor in detail.	8 Marks
	b.	Discuss the role of substrate in the MOS with relevant equations. NMOS transistor has $V_{t0} = 0.8\text{V}$, $2\phi_f = 0.7\text{V}$ and $\gamma = 0.4\text{V}^{1/2}$, find V_t when $V_{SB} = 3\text{V}$.	8 Marks
MODULE - 2			
3	a.	Draw the T – equivalent circuit model for the MOSFET and explain.	6 Marks
	b.	Explain the biasing of the MOSFET using constant current source.	6 Marks

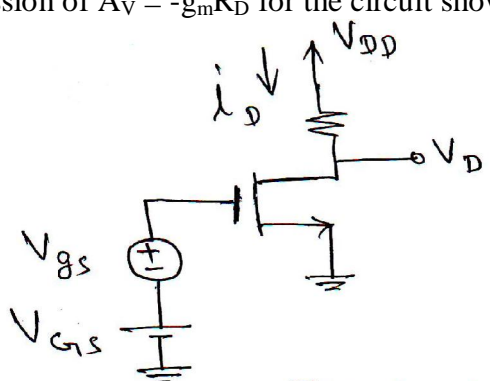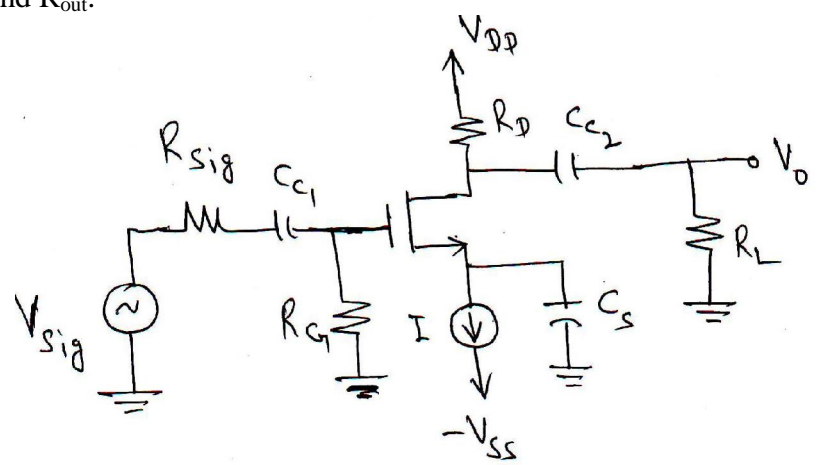	<p>c. Derive the expression of $A_V = -g_m R_D$ for the circuit shown in Fig. 3(c).</p>  <p style="text-align: center;">Fig. Q 3(c)</p>	4 Marks
--	--	---------

OR

4	<p>a. For the circuit shown in Fig. 4(a), obtain the expressions of R_{in}, A_V, A_{VO}, G_V and R_{out}.</p>  <p style="text-align: center;">Fig. Q 4(a)</p>	8 Marks
	<p>b. Explain the role of various internal capacitances in the MOSFET.</p>	8 Marks

MODULE - 3

5	<p>a. For an NMOS transistor with $W/L = 10$ fabricated in the $0.18\mu\text{m}$ process, find the values of V_{OV} and V_{GS} required to operate the device at $I_D = 100\mu\text{A}$. Ignore channel length modulation. Assume $\mu_n C_{OX} = 387\mu\text{A}/\text{V}^2$.</p> <p>b. Explain the operation of a basic MOSFET current mirror.</p> <p>c. State and prove the Miller's Theorem.</p>	<p>6 Marks</p> <p>5 Marks</p> <p>5 Marks</p>
---	---	--

OR

6	<p>a. Draw and explain the circuit for generating the number of constant currents of various magnitude of a current steering.</p> <p>b. Derive the expression for determining the 3-dB frequency (f_H) of an amplifier.</p>	<p>8 Marks</p> <p>8 Marks</p>
---	--	-------------------------------

MODULE - 4

7	<p>a. Draw the circuit diagram of a CMOS Common Source amplifier and explain its operation with the help of I-V characteristics and transfer</p>	8 Marks
---	--	---------

		characteristics.	
	b.	Explain what is Cascode amplifier and the basic idea behind the Cascode amplifier.	4 Marks
	c.	Explain the operation of a Double Cascoding.	4 Marks
OR			
8	a.	Draw the high frequency equivalent circuit model of the common source amplifier and explain the analysis using open circuit time constants.	8 Marks
	b.	Explain the effect of source resistance on transconductance and voltage gain of a CS- amplifier.	8 Marks
MODULE - 5			
9	a.	Explain the operation of MOS differential pair with a differential input voltage.	8 Marks
	b.	Obtain the expression of CMRR of an active loaded MOS differential amplifier.	8 Marks
OR			
10	a.	Draw the diagram of a two stage CMOS op-amp circuit and explain its operation.	8 Marks
	b.	Draw the frequency response of a differential amplifier due to variation of common - mode gain, differential gain and CMRR with frequency and analyse it.	8 Marks
