

Third Semester B.E. Degree Examination, Dec 2018

17EE 32ELECTRICAL CIRCUIT ANALYSIS


Time: 3 hrs.

MODEL PAPER Max. Marks: 100


Note: Answer FIVE full questions, choosing one full question from each module

Module – 1

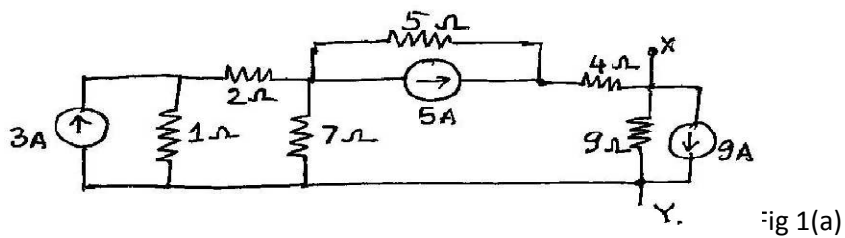
- 1 a. Perform source transformation and find a single voltage source in series with a resistance for the circuit shown in fig 1(a). 6 marks



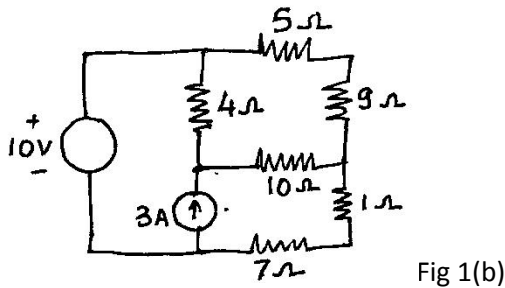- b. For the circuit shown in fig 1(b), solve for loop currents 6 marks




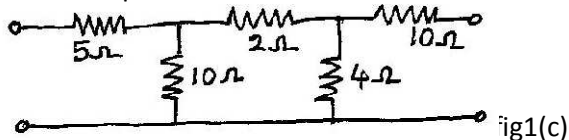- c. Find the equivalent delta connection for the circuit shown in fig 1(c). 8 marks



OR

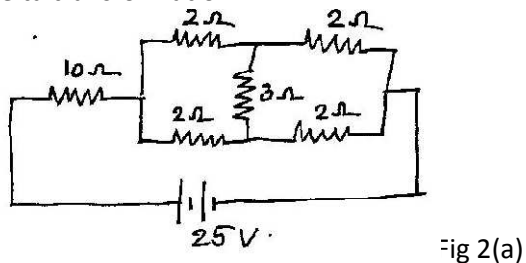- 2 a. Find the current in the 10 Ohm resistor for the circuit shown in fig 2(a). Use star delta transformation. 6 marks



- b. For the circuit shown in fig 2(b) determine all node voltages. 8 marks

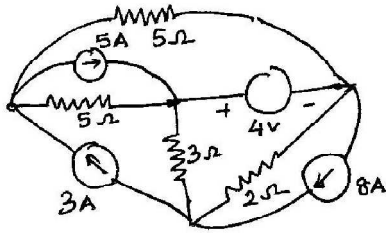


Fig 2(b)

- c. The node voltages equations for an electrical circuit are as follows:
Draw the circuit. 6 marks

Module – 2

- 3 a State and explain superposition theorem. 6marks
 b For the circuit shown in fig 3(b), find the Thevenin's equivalent circuit across X-Y terminals. 8 marks

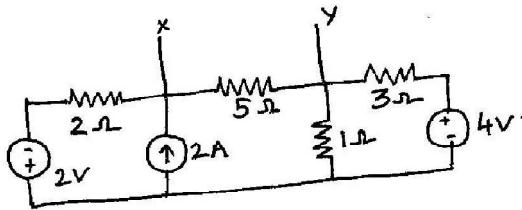


Fig 3(b)

- c For the circuit shown in fig 3(c), find the Norton's equivalent across X-Y terminals. 4 marks

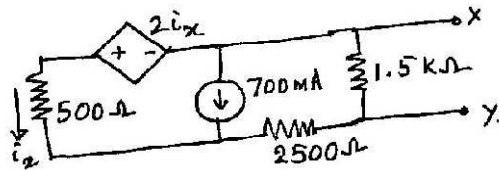


Fig 3 (c)

OR

- 4 a State and explain Norton's theorem 6 marks
 b In the network shown in fig. 4(b) determine the current I using superposition theorem. 8 marks

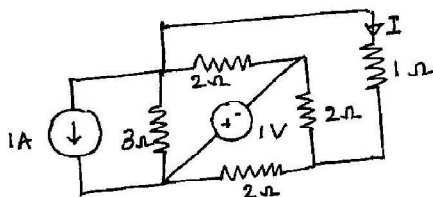


Fig 4 (b)

- c Find V_x and verify reciprocity theorem for the circuit shown in fig 4 (c) 6 marks

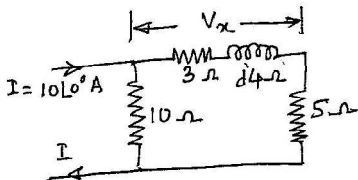


Fig 4 (c)

Module – 3

- 5 a A series R-L-C circuit is energized by a variable frequency AC supply. Derive the expressions for half power frequencies and bandwidth. 8 marks
 b For the circuit shown in fig 5(b) find the frequency at which the circuit will be at resonance. If the capacitor and inductors are interchanged, what will be the 6 marks

value of the resonance frequency?

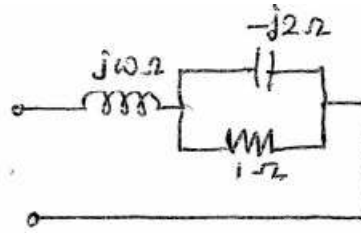


Fig 5(b)

- c Explain the behavior of circuit elements under switching action ($t = 0$ and $t = \infty$), 6 marks

OR

- 6 a Determine i , di/dt and d^2i/dt^2 at $t = 0+$ when the switch is moved from position 1 to position 2 in the circuit shown in fig.6(a) 8 marks

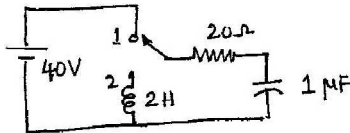


Fig 6 (a)

- b In a series RLC circuit, the resistance, inductance and capacitance are 10 ohms, 100 mH and 10 microfarad. Calculate ω_0 , ω_1 and ω_2 . Also find bandwidth and selectivity. 7 marks
- c Show that the circuit shown in fig 6 (c) resonant at supply frequency. 5 marks

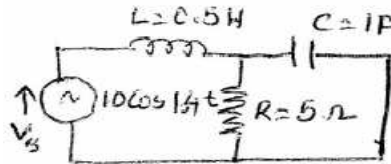


Fig 6(c)

Module – 4

- 7 a State and prove initial value and final value theorems 8 marks
- b Show that the Laplace transform of a periodic function is $1/(1 - e^{-Ts})$ times the Laplace transform of the first pulse. Where T is the period of the function. 6 marks
- c Obtain the Laplace transform of the pulse shown in fig. 7(c) 6 marks

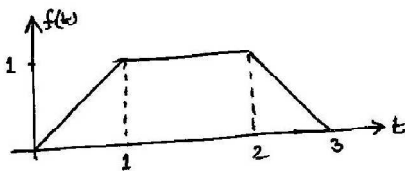


Fig 7(c)

- 8 a Determine the Laplace transform of half rectified sine wave of maximum value V 6 marks
- b Evaluate the Laplace transform of the periodic signal shown in fig. 8(b) 6 marks

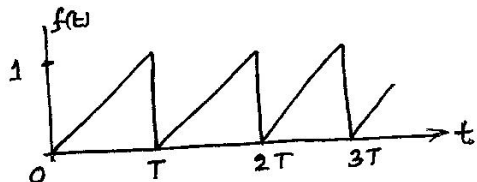


Fig 8(b)

- c Find the initial value and final value of the following functions: 8 marks
- (i) $I(s) = \frac{6.67(s+250)}{s(s+166.7)}$ (ii) $I(s) = \frac{s^3 + 7s^2 + 5}{s(s^3 + 3s^2 + 4s + 2)}$

Module – 5

- 9 a The delta connected load impedance shown in the fig.9(a) is supplied by a balanced 400 V three phase 50Hz supply. Phase sequence is RYB. Determine 8marks

the phase and line currents.

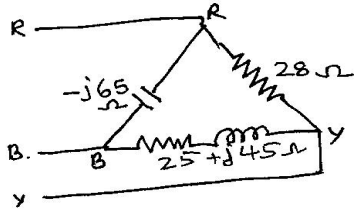


Fig 9 (a)

- b Find the z - parameters for the network shown in fig. 9 (b) 6 marks

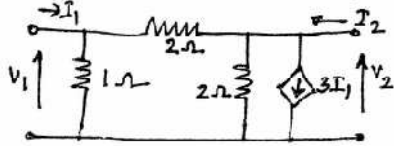


Fig.9 (b)

- c Find Y_{11} , Z_{21} , h_{21} and D from $2V_1 + 4 I_2 = I_1$

6 marks

$$8 I_2 = V_2 + 6V_1$$

OR

- 10 a For the network shown in fig. 10 (a), determine Y and Z parameters 8 marks

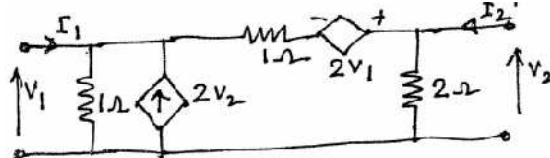


Fig.10 (a)

- b Given $I_1 = 0.25V_1 - 0.2 V_2$

4 marks

$I_2 = - 0.2V_1 + 0.1 V_2$ Find T - parameters

- c The unbalanced three phase 4 wire star connected load impedance shown in the fig.10(c) is supplied by a balanced 400 V three phase 50Hz supply. Phase sequence is RYB. Determine the voltage at the star point of the load with respect to supply neutral. Also determine the line currents.

8 marks

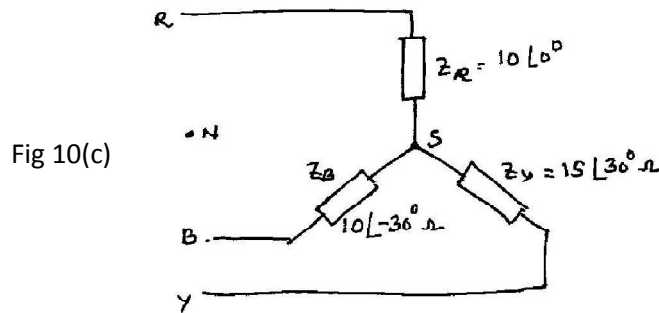


Fig 10(c)