Model Question Paper-I with effect from 2018-19

USN											17EE3
-----	--	--	--	--	--	--	--	--	--	--	-------

Third Semester B.E.(CBCS) Examination **Transformers and Generators**

(Core subject, E&EE)

Time: 3 Hrs Max.Marks: 100

Note: Answer any FIVE full questions, choosing at least ONE question from each module.

Module-1

- 1. (a) Draw and explain the full load phasor diagrams of single phase transformer for lagging, leading and unity power factor loads. (07 Marks)
 - (b) Write a short note on "All day efficiency of a transformer". **(05 Marks)**
 - (c) Starting from the fundamentals, develop the equivalent circuit, exact equivalent circuit and approximate equivalent circuit of a 1- Ø transformer referred to primary side. **(08 Marks)**

OR

- 2. (a) State the advantages of single 3-Phase unit transformer over bank of single phase transformers. **(06 Marks)**
 - (b) With the help of phasor diagram, explain how 2 phase supply can be obtained from 3 phase supply using Scott connection. **(08 Marks)**
 - (c) A 4 kVA, 200/400V single phase transformer supplying full load current of 0.8 p.f lagging. The OC/SC test results are:

OC Test: 200V, 0.8A, 70W.

SC Test: 20V, 10A, 60W (HV side). Calculate the efficiency.

(06 Marks)

Module-2

- 3. (a) With a circuit diagram explain in detail Sumpner's test for determining the efficiency and voltage regulation of transformer. **(08 Marks)**
 - (b) Discuss the necessary conditions for the parallel operation of two transformers.

(04 Marks)

(c) Derive an expression for the currents shared between the 2 transformers connected in parallel supplying a common load when no load voltages of these transformers are unequal. **(08 Marks)**

OR

- **4.(a)** Two transformers each of 800kVA are connected in parallel. One has a resistance and reactance of 1% and 4% respectively and the other has resistance and reactance of 1.5% and 6% respectively. Calculate the load shared by each transformer and corresponding power factor when the total load shared is 100 kVA at 0.8 p.f lagging.
- (b) What is an auto-transformer? Derive an expression for the saving of copper in an auto-transformer as compared to an equivalent two winding transformer. (07 Marks)

(Page 1 of 2)

(c) With the help of sketches, explain the working of ON load tap changer and OFF load tap changer. **(08 Marks)** Module-3 **5.** (a) Explain the necessity of tertiary winding transformer. **(06 Marks) (b)** How stabilization is achieved due to tertiary winding.? (06 Marks) (c) With a neat circuit diagram, explain armature reaction in DC machines. **(08 Marks) 6.** (a) What is commutation? With a neat diagram, explain the process of commutation. **(07 Marks)** (b) Define pitch factor and distribution factor of an synchronous generator and derive an expression for distribution factor K_d and pitch factor K_p in synchronous generator. **(08 Marks)** (c) Explain the methods used to reduce harmonics in synchronous generator. (05 Marks) Module-4 7. (a) What is synchronization of alternators? Explain the need for parallel operation of alternators. **(08 Marks) (b)** Define electrical load diagram of a synchronous generator. **(04 Marks)** (c) With a phasor diagram, explain the concept of two reaction theory in a salient pole synchronous machine. **(08 Marks)** OR **8.** (a)Discuss the effect of change of excitation at constant load. **(06 Marks) (b)**Write a note on V curve of synchronous generator. **(06 Marks)** (c) With a neat circuit diagram, explain the slip test on salient pole synchronous machines and indicate how X_d and X_q can be determined from the slip test. **(08 Marks)** Module-5 9. (a) Define voltage regulation of an alternator. What are the various methods of determining the voltage regulation for 3- Ø alternator and explain anyone method in detail. **(10 Marks)** (b) A 2300 V, 50 Hz, 3 phase star connected alternator has an effective armature resistance of 0.2Ω . A field current of 35A produces a current of 150 A on short circuit and an open circuit emf 780 V (line). Calculate the voltage regulation at 0.8 pf lagging and 0.8 pf leading for the full load current of 25A. (10 Marks) **10.** (a) Explain the capability curves of synchronous generator. **(07 Marks)** (b) Discuss about hunting in synchronous machines. Also explain the role of damper **(07 Marks)**

(Page 2 of 2)

(06 Marks)

(c) Discuss about short circuit ratio and its significance.
