

18ELN14/24

Visvesvaraya Technological University, Belagavi

MODEL QUESTION PAPER

1st/2nd Semester, B.E (CBCS 2018-19 Scheme)


Course: 18ELN14/24- BASIC ELECTRONICS - **Set no.1**


Time: 3 Hours

Max. Marks: 100

Note: (i) Answer Five full questions selecting any one full question from each Module.

(ii) Question on a topic of a Module may appear in either its 1st or/and 2nd question.
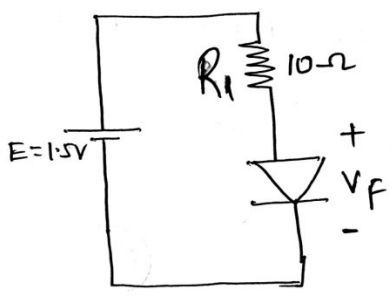
| | | Module-1 | Marks |
|---|---|--|-------|
| 1 | a | Explain the operation of p-n junction diode under forward and reverse biased condition | 8 |
| | b | Explain how Zener diode can be used as a voltage regulator | 6 |
| | c | A diode circuit shown below has $E=1.5V$, $R_1=10\ \Omega$. By assuming $V_f=0.7V$, calculate I_f for i) $r_d = 0$ ii) $r_d = 0.25\ \Omega$ | 6 |
| | |  <p>Fig.Q.1(c)</p> | |
| | | OR | |
| 2 | a | With a neat circuit diagram and waveform, explain the working of half-wave rectifier and derive the expression for average load current. | 8 |
| | b | Explain briefly the operation of a capacitor filter circuit. | 6 |
| | c | Explain the operation of 7805 fixed IC voltage regulator. | 6 |
| | | Module-2 | |
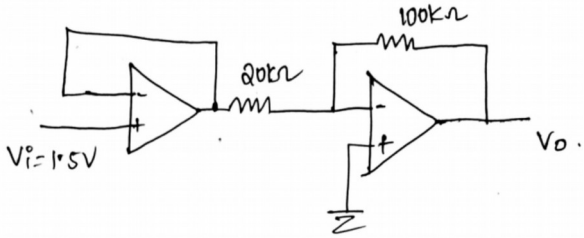
| | | | |
|---|---|--|---|
| 3 | a | Explain the characteristics of N-channel JFET. | 8 |
| | b | For E-MOSFET, determine value of I_D , if $I_D(ON) = 4\text{mA}$, $V_{GS}(ON) = 6\text{V}$, $V_T = 4\text{V}$ and $V_{GS} = 8\text{V}$. | 4 |
| | c | Explain the construction and working of P-channel enhancement type MOSFET. | 8 |
| | | OR | |
| 4 | a | Draw and explain the operations of SCR using 2-transistor equivalent circuit. | 8 |
| | b | Explain phase controlled application of SCR. | 6 |
| | c | Explain the operation of a CMOS inverter. | 6 |
| | | Module-3 | |
| 5 | a | For an op-amp (i) List the characteristics of an ideal op-amp and (ii) Draw the three input inverting summer circuit and derive an expression for its output voltage. | 8 |
| | b | Define the terms i) Slew rate ii) CMRR iii) Common mode gain A_c of op-amp | 6 |
| | c | Design an adder circuit using an op-amp to obtain an output voltage of $V_o = -[2V_1 + 3V_2 + 5V_3]$ | 6 |
| | | OR | |
| 6 | a | Draw the working of an inverting op-amp. Derive the expression for its voltage gain. | 8 |
| | b | With a neat diagram, explain how an op-amp can be used as a differentiator. | 6 |
| | c | Find the output V_o of following op-amp circuit.  <p style="text-align: center;">Fig.Q.6(c)</p> | 6 |

| Module-4 | | | |
|-----------------|---|---|---|
| 7 | a | Explain the operation of BJT as an amplifier and as a switch. | 8 |
| | b | What is a feedback amplifier? Briefly explain different types of feedback amplifiers. | 6 |
| | c | Draw and explain the operation of a voltage series feedback amplifier and derive an expression for its voltage gain with feedback. | 6 |
| OR | | | |
| 8 | a | Explain the Barkhausens' criteria for oscillations. | 6 |
| | b | Explain the operation of an RC phase shift oscillator. | 6 |
| | c | Explain the working of an Astable oscillator constructed using IC- 555 timer. | 8 |
| Module-5 | | | |
| 9 | a | Convert the following. i) $(725.25)_{10} = (?)_2 = (?)_{16}$ ii) $(111100111110001)_2 = (?)_{10} = (?)_{16}$ | 8 |
| | b | Simplify the following expressions and draw the logic circuits using basic gates. i) $AB + \bar{A}C + A\bar{B}C$ ($AB+C$) ii) $(A+\bar{B})(CD+E)$ | 6 |
| | c | Realize a full adder circuit using 2 half adders. | 6 |
| OR | | | |
| 10 | a | What is a multiplexer? Explain the working of 4:1 multiplexer. | 6 |
| | b | With the help of a logic diagram and truth table, explain the working of a clocked SR flip-flop. | 6 |
| | c | What is a shift register? Explain the working of a 4-bit SISO shift register. | 8 |
